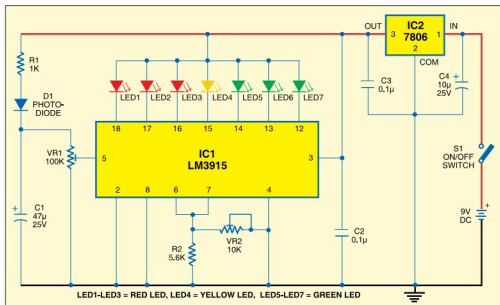




ing preset VR2 you can set the lower limit of the light intensity at which the first LED (LED1) should light up. By varying preset VR1 you can set the input voltage to the IC for the upper limit at which LED7 should light up. LED1 indicates minimum light, LED4 (yellow) indicates moderate light and LED7 indicates normal light. Capacitor C1 provides a slight lag to turn on/off each of the LEDs.

Assemble the circuit on a general-purpose PCB and enclose in a suitable cabinet.

When adjusting VR1, the wiper of VR2 should be fully turned in the clockwise direction.

EFY note. The circuit will not work in fluorescent lighting, as it is a pseudo light without monochromatic spectrum. ●

the LED scale. Each LED from pin 18 downwards lights up when input pin 5 of IC1 receives an increment of 1.25 volts. Internally, the IC has ten comparators with a current source output, plus a reference and ladder

der voltage divider that provides necessary reference voltage. Pin 7 of the IC is maintained at a reference voltage of 1.25 volts and resistor R2 controls current through the LEDs and thus their brightness. By vary-

Tell Me More About Advertising Opportunities in EFY Magazine

I am aware that EFY Magazine presents umpteen advertising opportunities. I too would like to explore the various options available for my organisation, so that I can help it grow in terms of sales and brand presence. My details are mentioned below:

Name _____
 Organisation _____
 Designation _____
 Address _____
 City _____ Pincode _____
 Phone _____ Fax _____
 E-mail _____

I would like to have a one-to-one meeting

- ☐ I would like to have a one-to-one meeting with someone from the EFY team.
☐ Please send me your marketing kit containing all necessary details.

Please mail/fax this form to:



EFY Enterprises Pvt Ltd

D-87/1, Okhla Industrial Area, Phase-I, New Delhi 110020

Tel: 011-26810601/2/3; Fax: 011-26817563

Email: efymkt@efyindia.com; Website: www.efyindia.com