

to launch the audio recording software and start recording.

For phone recording, simply connect the stereo jack to the AUX IN port of the PC. Install the Audacity audio recorder (different versions are available for free for different operating systems at <http://audacity.sourceforge.net/>) on your PC. Run the executable Audacity file. In the main window, you will find a drop-down box in the top right corner. From this box, select the AUX option. Now you are ready to record any call. As soon as a call comes in,

press the record button found in the Audacity main window and then pick up the telephone receiver and answer the call. Press the stop button once the call ends. Now go to the file menu and select the 'Export as WAV' option and save the file in a desired location.

You may change the value of resistor R2 if you want to change the output volume. You can use a variable resistor in series with R2 to vary the volume of the output. The recorded audio clip can be edited using different options in the Audacity software.

You can assemble the circuit on a general-purpose PCB and enclose it in a small cabinet. Use an RJ11 connector and stereo jack for connecting the telephone set and computer (for call recording). Telephone cords can be used to connect to the phone line and the circuit. Use of a shielded cable is recommended to reduce disturbances in the recording. These can also be reduced by increasing the value of R2 to about 15 kilo-ohms.

EFY note. Audacity recording software is included in this month's EFY-CD under 'Utilities' section. ●

ELECTRONIC QUIZ SWITCH

■ P. SIDDEEQ BASHA

One of the common rounds in the quizzes is the buzzer round. We are describing here a simple electronic circuit that can

be used in any test or quiz competition. In this circuit, only four persons can participate, and every participant is assigned a certain number. Whenever a switch is pressed, the circuit locks the remaining three entries. At the same

time, an alarm sounds and the designated switch number is displayed on the 7-segment LED display.

When a player presses his switch, the corresponding output of IC1 goes

