

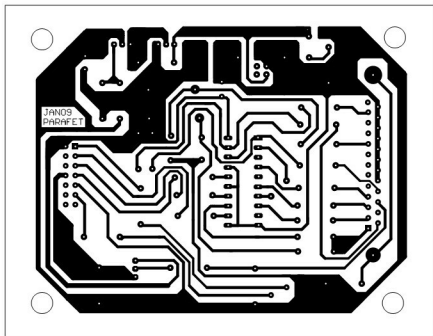


Fig. 7: A single-side, actual-size PCB layout for ParaFET circuit shown in Fig. 6

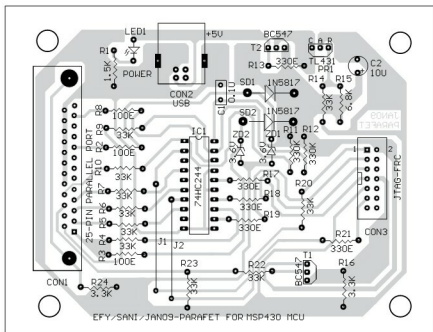


Fig. 8: Component layout for the PCB

Construction

The ParaFET circuit components can be accommodated on a single-side PCB. All the components used in the circuits including the ParaFET, blinking LED and thermometer have been listed in the parts list above. An actual-size, single-side PCB layout of the ParaFET circuit is shown in Fig. 7 and its component layout in Fig. 8.

Once the components are soldered, the board can be connected to the PC's parallel port.

The 25-pin parallel-port connector should be a female connector mounted on the PCB board. Attach the body of the female connector to the PCB board firmly. Connect it to ground line of the circuit through a 3.3-kilo-ohm resistor, P1 and P2 shown in the circuit are nothing but the connecting points of the metallic part of connector CON1 to the PCB board. A 25-pin FRC cable about 40cm in length with 25-pin parallel-port male connector at both ends can be used to connect the circuit board and the PC.

A 14-pin FRC cable about 20cm in length with 14-pin header (female) at both ends can be used to connect the target board from the JTAG connecting points. An industry-standard USB cable is required to connect the PC when extra power is required in the target board. Glowing of LED1 indicates that the board is connected to the PC.

After you have successfully assembled the circuit, however, without invoking the IAR IDE tool and connecting a target board to the ParaFET, not much can be tested. The next section will describe building the target board for testing the working of the ParaFET.

To be concluded next month...



Become a LINUX Pro

set up Web servers, email servers,
fax gateways...

Read LINUX For You

ASIA'S FIRST
LINUX MAGAZINE

For more info, log on to:
www.linuxforu.com