 


The charging cycle repeats to give a flashing effect in the bulb. The 'on' time of the flasher is controlled by the



The signal flasher is a four-bulb system as shown in Fig. 2. Two bulbs are used at the front of the vehicle and the other two at the back of the vehicle. The primary function of the 'turn' signal flasher is to flash the lamps when the 'turn' signal switch is activated to




The circuit of the hazard-warning flasher is shown in Fig. 3. Used in vehicle lighting systems, it flashes all the four bulbs when hazard-warning switch S3 is 'on.' During hazard warning, switch S2 can be in the left or right position.

The alternate flasher circuit is shown in Fig. 4. It flashes the lamps alternately when the system is activated. This type of flasher is typically used in emergency vehicles and school buses. ●

This is a very useful device for those who are frequently on the move. It will keep your tea, coffee or food warm while consuming little power.

 ected in reverse direction to facilitate maximum variation of the duty cycles.



S1-S4 = 5A. ON/OFF SWITCH

Power transistor T1 is Darlington type with 5A capacity and output of more