

the respective door (1). At the same time, piezobuzzer PZ1 sounds.

Construction

Actual-size, single-side PCBs for the door unit (Fig. 1) and the control unit (Fig. 2) of the multichannel door alarm with display are shown in Figs 3 and 5 and their component layouts in Figs 4 and 6, respectively.

After mounting all the components on the PCB, connect the door unit (say, Door 1) via a three-core cable to the corresponding point (Door 1) of the control unit. Nine door-unit PCBs are required for the nine doors. Mount a small magnet at the opening shutter of the door, and the door unit on the door frame (fixed side of the door).

When the door is closed, the magnet comes near the reed switch and the reed switch closes. When the door is opened, the reed switch opens. Close the door after fitting the magnet and the door unit, then press the reset switch. The LED of the door unit turns off and the connected relay de-energises. As a result, the display shows '0.'

When any of the doors (say, sixth door) is opened, the LED connected

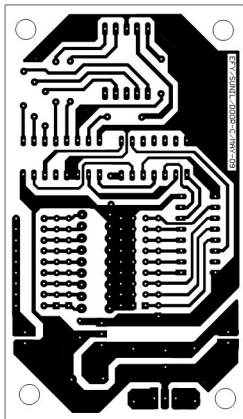


Fig. 5: Actual-size, single-side PCB for the control unit of multichannel door alarm with display

at the respective door unit glows and relay RL6 energises. The display shows '6' and simultaneously the buzzer sounds, alerting you that door No. 6

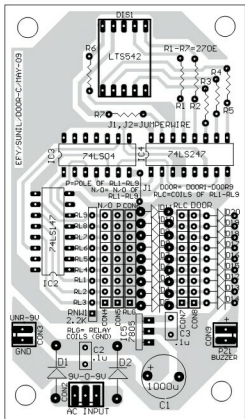


Fig. 6: Component layout for the PCB shown in Fig. 5

has been opened. This way the multichannel door alarm works for each of the doors and discourages the intruders to enter your house. ●

Few of the topics that we have already covered...

- How to Make Diskless PCs
- How to Setup a Web Server
- A Fully-fledged Email Server



Read **LINUX For You**

For more info, log on to: www.linuxforu.com

ASIA'S FIRST
LINUX MAGAZINE



LINUX
THE COMPLETE MAGAZINE ON LINUX SYSTEMS
For You