



This PIC16F877A microcontroller-based quiz controller, designed for up to six players or teams, is suitable for school and college quiz competitions. It is similar to a fastest-finger-first system in which the player who presses the button first gets the first chance to answer the quiz.

Here, each team is assigned a unique number and provided with a pushbutton switch. As soon as a ques-

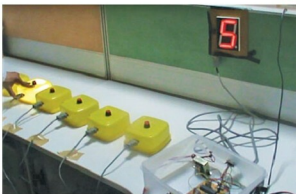


Fig. 1: Author's prototype

tion is asked by the quiz master, any of the participating teams can press the button and give the answer within the allotted time. A buzzer sounds and a big 12.7cm (5-inch) 7-segment display shows the number of the team that presses their pushbutton switch first. Author's prototype is shown in Fig. 1.

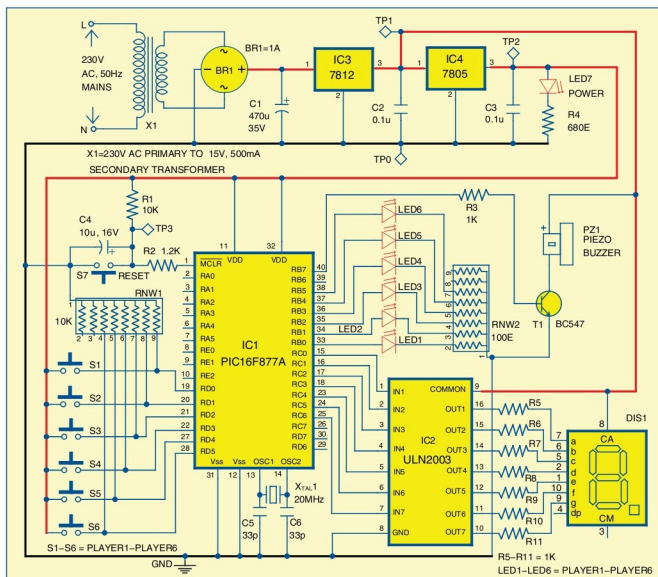


Fig. 2: Circuit diagram of the quiz controller