

Fig. 2: Actual-size PCB layout for the audio amplifier circuit

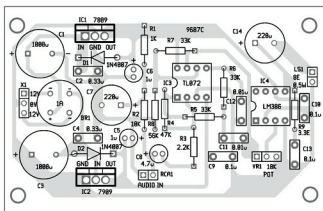


Fig. 3: Component layout of the PCB

listened-to through the speaker (LS1). Potentiometer VR1 is used for volume control.

Construction and testing

An actual-size, single-side PCB for the simple low-power amplifier is shown in Fig. 2. Its component layout is shown in Fig. 3. After assembling the circuit on the PCB, enclose it in a suit-

able plastic box.

Fix RCA1 socket on the front side of the box for an audio-in signal. Fix a three-pin connector on the PCB for connecting secondary terminals (12V-0-12V) of transformer X1 and to two-pin connector on the rear side for mains 230V AC, 50Hz. Fix the transformer firmly on the cabinet with screws or nuts and bolts. Con-

nect the speaker affixed on top of the box or placed at a distance. Use a shielded cable for connecting to the RCA socket.

Before inserting IC3 and IC4 into their respective IC bases, verify that all the connections have been made properly. ●

The author is a lab engineer at EFY

www.pcbpower.com

PCB[®]
Power

What is New?



Free DFM check
of your data for better
manufacturability



Design solutions
PCB Design services
& Design Software



Soldering Equipments
for small quantity
SMD-PCB assembly

- ✓ Students
- ✓ Hobbyists
- ✓ Designers

- ✓ Automotive
- ✓ Industrial
- ✓ R & D

- ✓ Railway
- ✓ Telecom
- ✓ Space



Call us @ 7600012414 & 7600012415
E-mail - sales@pcbpower.com

Online PCB Specialist

- PCB Up to 24 layers
- High Frequency (RF) PCB
- No Minimum Order Value
- Minimum Order Quantity : 1
- No Tooling Charges
- Delivery 24hrs onwards
- Online Quotes & Tracking
- 24Hrs. Online Assistance
- SMS Update services
- Fast & Reliable Logistic

Circuit Systems India Ltd.

B-24, GIDC, Electronics Estate, Sector-25,
Gandhinagar-382044, Gujarat, India