

Fig. 2: An actual-size PCB layout for the driver circuit

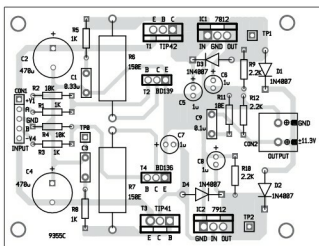


Fig. 3: Component layout for the PCB

We should use an appropriate voltage converter to drive the signal from TTL/CMOS signals. With appropriate additional logic the signals at points A and point B are controlled with one TTL/CMOS signal.

In brief, when signal at A is high, you get $+12V - 0.7V = +11.3V$ at CON2 and when signal at B is low (negative), you get $-12V + 0.7V = -11.3V$ at CON2.

Construction and testing

An actual-size, single-side PCB for the peripheral driver with fixed regulators 78xx and 79xx is shown in Fig. 2 and its component layout in Fig. 3. After assembling the circuit on PCB, enclose it in a suitable plastic box. Fix 5-pin connector CON1 for input signal and 2-pin connector CON2 for output. A

suitable common heatsink may be used for T1 and IC1. The same for T3 and IC2.

Before inserting the load, first verify that the test point voltages are as per table. ●

The author was a researcher and assistant professor in Technical University of Sofia (Bulgaria) and expert-lecturer in OFPPT (Casablanca), Kingdom of Morocco. Now he is working as an electronics engineer in the private sector in Bulgaria



Would You Like More Hands-on Circuits?

We Have Thousands!

VISIT TODAY

electronicsforu.com

If it's electronics, it's here