



Fig. 4: Connections of home-made on/off circuit inside APC's 800VA inverter

The primary side of the transformer is connected to 230V AC input line of the inverter. The 12V-0-12V, 250mA secondary output of the transformer is rectified by two diodes, filtered by a

1000 μ F, 35V capacitor and regulated by IC 7812. The 12V regulated output is fed to a 12V change-over relay through which the switching action takes place.

When the 230V AC mains is

available, the relay energises and its common pole shifts to the normally-open (N/O) contact. The 230V AC output from the inverter is not available at its output socket. When mains goes off, the relay de-energises and its pole shifts towards the normally-closed (N/C) contact. The 230V AC output from the inverter is now available through the N/C contact. Fig. 4 shows connection of the on/off switching circuit to the main inverter circuit.

If the inverter output load is known, this simple circuit can be inserted in any home inverter for auto-on/off switching. For a higher load, use a relay having a higher current rating. ●

Kshatij

27th - 30th January 2012

ASIA's **LARGEST**
techno-management fest

Events

Exhibitions

Workshops

Megashows

Guest Lectures

www.ktij.in

Strategic Partners

Major Sponsors

Event Sponsors

Media Partners

Other Sponsors