

Fig. 3: An actual-size, single-side PCB for cellphone-based remote controller

Construction and testing

An actual-size, single-side PCB for cellphone-based remote controller is shown in Fig. 3 and its component layout in Fig. 4. Suitable connector is provided on the PCB to connect the cellphone. Assemble the circuit on a PCB to minimise time and assembly errors. Carefully assemble the components and double-check for

any overlooked error. Use suitable IC socket for MT887 and NE555 ICs.

Use relay RL1 with contact current rating capable of carrying the water pump's current.

To test the circuit for proper functioning, press switch S1 and verify 5V at TP1 with respect to TP0. Connect the cellphone to the controller using con-

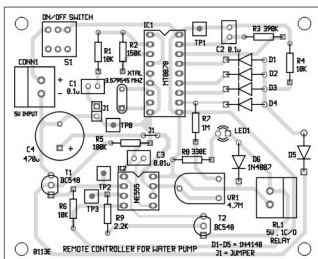


Fig. 4: Component layout for the PCB

ductor J1. Call this cellphone and press '7' once the ring stops. At the same time, verify high-to-low triggering pulse at TP2. TP3 now should be high for the preset time period. ●

The author is a final year B.Tech (electrical and electronics engineering) student at MG University. His areas of interest include embedded systems and power electronics

SanRex

LEADING THE NEW POWER ELECTRONICS ►►

Power semiconductor

- TRIAC
- THYRISTOR
- DIODE, FRD, SBD

DCAUTO F series

~ high-powered plating for electronic parts

MRT series

(500A-3000A)
~ Inverter power supply for various plating

Grid Connected Photovoltaic Central Inverter

Our official agencies in India are as follows:

Semi-conductor Peif Electronics Pvt. Ltd. TEL +91-20-324 00389 SETSUYO ASTEC SINGAPORE PTE. LTD. INDIA LIAISON OFFICE TEL +91-11-416 74491	Power Source Equipment SETSUYO ASTEC SINGAPORE PTE. LTD. INDIA LIAISON OFFICE TEL +91-11-416 74491
--	--

SANSHA ELECTRIC MFG. CO., LTD.

SANREX ASIA PACIFIC PTE.LTD.
25, Tagore Lane, #03-12A, Singapore Godown, 787602, Singapore
TEL +65-6487-8687, +65-6488-6428 FAX +65-6489-6428 Email: admin@sanrex.com.sg

www.sansha.co.jp/official/englishsite/