

Remote Control Using Wireless Doorbell



RAJ K. GORKHALI

This circuit lets you wirelessly control an appliance from a remote place by using a wireless doorbell. The appliance is triggered by the signal from the transmitter of the wireless doorbell and turns off automatically after the preset time period.

Circuit and working

The circuit comprises a doorbell (DB1), timer NE555 (IC1) and a few discrete components. The audio output from the battery-powered doorbell receiver is connected to series resistor R1, then AC coupled to the base of npn transistor BC548 (T1) using capacitor C1 and resistor R2.

Test Point Details

Test point	Details
TP0	GND
TP1	12V (when switch S1 is 'on')
TP2	Triggering pulse for timer IC1
TP3	12V (load enabled)

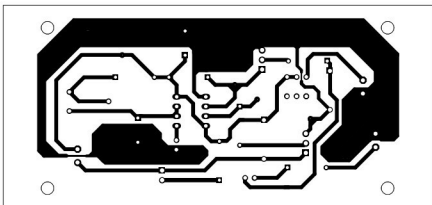


Fig. 2: An actual-size, single-side PCB for the remote control using wireless doorbell

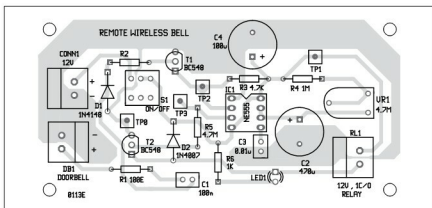


Fig. 3: Component layout for the PCB

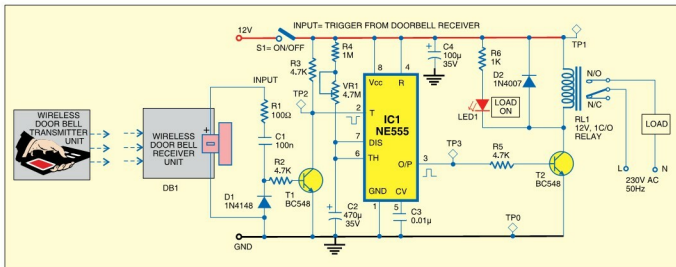


Fig. 1: Circuit of remote control using wireless doorbell