

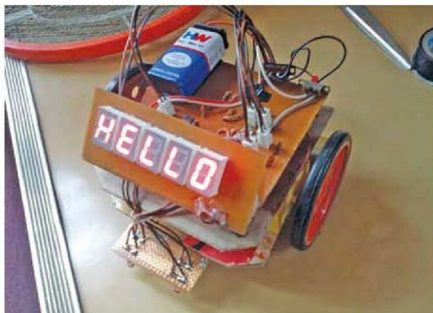


Fig. 8: Author's prototype

the front of the robot with both the sensors facing towards the ground. Distance between the right and left sensors should be aligned properly

as per the width of the track on the ground.

Assemble the circuit on a PCB as it minimises time and assembly

errors. Carefully assemble the components and double-check for any overlooked error. Use of IC bases for IC3 and IC4 is recommended. Before putting the ICs, always check the correct supply voltage. Suitable connectors are provided on the PCB to connect geared motors M1 and M2 and sensors IC1 and IC2. Connect the motors and power the circuit with a 12V battery. Place the robot on the track. Sensors sense the white or black track on the surface and the robot follows that track. A 'hello' message can be displayed on top of the robot by using the circuit shown in Fig. 5. An actual-size, single-side PCB for Fig. 5 is shown in Fig. 6 and its component layout in Fig. 7. Working prototype photograph is given in Fig. 8. ●

The author is a BE final-year student of information technology. His interests include electronics and robotics, website designing, software development and microcontrollers.

AN
EFYGROUP
MAGAZINE

8 Keys That You Can Press

E F Y T I M E S

To Stay Abreast With The Latest Technology News!

If IT's Technology, IT's Here!

Start Now

- Electronics
- Infotech
- Linux & Open Source
- Consumer Electronics
- Telecom
- Mobiles
- BPO
- Science & Technology
- and more

