

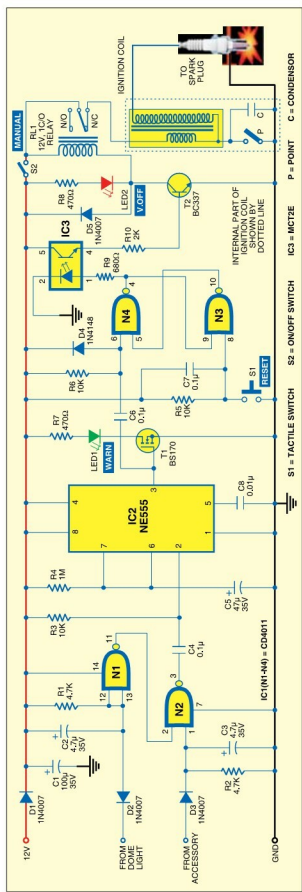


Fig. 1: Circuit of anti-carjack system

insulated wires for these connections.

Preliminary test. You need a 12V DC source, two SPST switches and a multimeter for preliminary testing of the circuit. One SPST switch (say, switch-1) is connected between the dome light and ground and the other SPST switch (say, switch-2) is connected between the accessory point and 12V.

Check the circuit for proper connection and polarity. Also, make sure that both SPST switches are open. Now turn the power 'on.' If LED1 glows, allow at least 60 seconds for it to go 'off.' If LED2 glows, press reset switch S1 to put it off.

Close test by connecting to ground. Both LEDs should go off. Open test switch-1, then close test switch-2 to simulate ignition 'on' condition. Both LEDs should remain 'off.' Close both test switches (switch-1 and switch-2), then open them. LED1 should glow. It should continue to

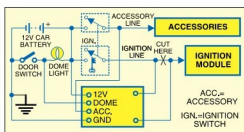


Fig. 2: Wiring diagram

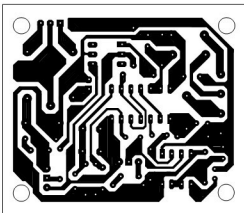


Fig. 3: An actual-size, single-side PCB for the anti-carjack system

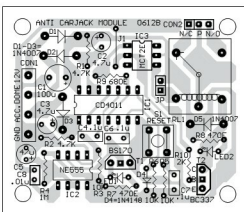


Fig. 4: Component layout for the PCB

glow for about 60 seconds. When LED1 goes off, LED2 should light up. Use multimeter to verify the resistance between the N/C contact and the pole of relay RL1. It should be infinite. Now if you press reset switch S1, LED2 should go off.

If the circuit performs as described above, the system is ready to install in your vehicle.

Installation. Before installing the anti-carjack module in the vehicle, locate the wires that you will need to connect the unit (refer Fig. 2). Trace