

SANI THEO

Here we present the circuit of an electronic chanting device having nine bhajans and one mantra to choose from. They are jai ganesh jai ganesh jai ganesh deva, jai jai jai jai ambe rani jai bhavani, jai matadi jai matadi, om namah shivaya om namah shivaya (mantra), radhe krishna radhe shyam, govind bolo hari gopal bolo, shriraman narayan narayan narayan, shri ram jai ram jai ram jai jai jai jai jai siyaram, jai jai jai jai jai hanumaan and jai jai jai jai jai siyaram jai jai jai jai jai hanumaan.

The device is small and handy to carry anywhere and can be used while traveling. It is ideal not only for the *pooja* room but could be kept in the living room also—a suitable gift for any occasion.

Circuit and working

The *bhajan* and *mantra* chanting amplifier circuit is shown in Fig. 1. It is powered by a 9V PP3 battery. The circuit is built around a chip-on-board (COB) and LM386 audio amplifier (IC1). The chanting IC (COB1) is available as Ganapati 10x1 in the Indian market. Zener diode provides 3.3V to COB1 for its operation. The prerecorded ten songs are already stored in COB1. Resistor R2 connected at pin 2 of COB1 is the

element to generate appropriate sound frequency in the COB. Audio output is available at pin 9 of the COB.

Test Points

Test point	Details
TP0	GND
TP1	9V
TP2	3.3V
TP3	2V (RMS)
TP4	3.5V (RMS) at full volume

PARTS LIST

Semiconductors:

- | | |
|------|-----------------------------------|
| IC1 | - LM386 low-power audio amplifier |
| COB1 | - Ganpati 10×1 chip-on-board |
| ZD1 | - 3.3V zener diode |

Resistors (all 1/4-watt, $\pm 5\%$ carbon):

- R1 - 120-ohm
R2 - 220-kilo-ohm
R3 - 10-ohm
VR1 - 10-kilo-ohm potentiometer

Capacitors:

- | | |
|----|---------------------------------|
| C1 | - 22 μ F, 25V electrolytic |
| C2 | - 10 μ F, 25V electrolytic |
| C3 | - 100 μ F, 25V electrolytic |
| C4 | - 220 μ F, 25V electrolytic |
| C5 | - 1 μ F, 25V electrolytic |
| C6 | - 0.1 μ F ceramic |

Miscellaneous:

- LS1 - 8-ohm, 0.5W loudspeaker
S1 - On/off toggle switch
- 9V PP3 battery

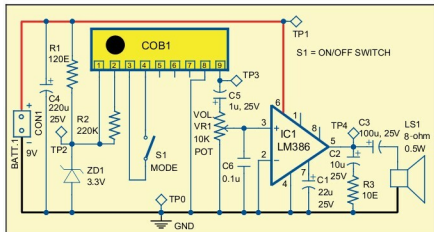


Fig. 1: The bhajan and mantra chanting amplifier circuit

ELECTRONICS
BAZAAR

INDIA'S FIRST ELECTRONICS SOURCING MAGAZINE

COMPONENTS. PRODUCTS. MACHINERY.

ELECTRONICS BAZAAR
The Great **SURVIVAL**
EMS Industry Focus Reformation

SINGODIA
THE PROFESSIONAL EX-CELSION