




The most important design aspect

Test point	Details
TP0	0 V, GND
TP1	+12 V
TP2	-12 V
TP3	Full rectified wave
TP4	Sawtooth wave
TP5	Sharp pulses (both positive and negative)
Across G1 and K1	Pulse (only positive)
Across G2 and K2	Pulse (only positive)

This basic circuit can be extended to higher values of voltages and load currents, by using suitably rated SCRs and power transformers.

The pulse generator section generates SCR triggering pulses synchronised with the input sine wave. It is built around transformer X1, bridge rectifier BR1, quad operational amplifier LM324 (IC1), +15V voltage regulator 7815 (IC2), -15V voltage regulator 7915 (IC3), pulse transformer (X3), npn

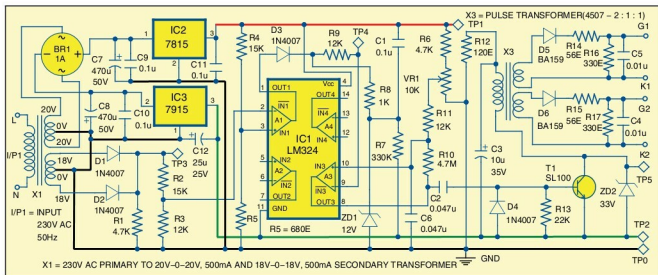Note. The remaining components are based on your design and requirements



WWW.FEYMAG.COM