



Fig. 2: An actual-size, single-side PCB for the wireless FM microphone

can be easily heard through the FM receiver if it is within the range of around 45m.

Construction and testing

An actual-size, single-side PCB for the wireless FM microphone is shown in Fig. 2 and its component layout in Fig. 3. After assembling the circuit on PCB, enclose it in a suitable plastic box. Fix speaker LSI on the front side and the

battery at the back side of the box.

Variable capacitor VC1 (used for tuning) may also be soldered directly on the top side of the first and last coil turns and fixed such that it can be adjusted through a small hole drilled in the box. The antenna may be mounted using a soldering lug between the mounting screw and the plastic box. The lug serves as the antenna connector. Mount miniature potentiometer

