

Fig. 2: An actual-size, single-side PCB for the voice recorder and playback system

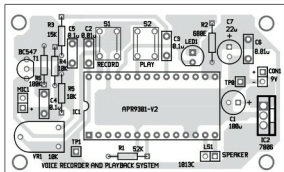


Fig. 3: Component layout for the PCB

1. 38 kilo-ohms for 16 seconds
2. 52 kilo-ohms for 20 seconds
3. 67 kilo-ohms for 24 seconds
4. 75 kilo-ohms for 30 seconds

Playback mode. When switch S2 is pressed momentarily, the recorded message plays from the start and can be heard from speaker LS1.

Standby mode. Pin 6 of IC1 is kept 'low' so that it returns to standby mode after the completion of recording and playback. If pin 6 is high, it will be in power-down mode and no recording or playback is allowed and current consumption is typically less than 1 μ A.

Working of the circuit

is simple. You can record your message for the duration defined by resistor R1 by keeping switch S1 pressed. Once recorded, the message can be played simply by pressing switch S2 momentarily.


Construction and testing

An actual-size, single-side PCB for the voice recorder and playback system is shown in Fig. 2 and its component layout in Fig. 3. Suitable connectors are provided on the PCB for connecting the microphone and speaker. Assemble the circuit on the provided PCB to minimise assembly errors. Carefully assemble the components and double-check for any overlooked error.

The circuit is simple and doesn't need many test points to verify. Check the correct power supply at TP1 with respect to TP0. Press switch S1. If LED1 glows, it implies IC1 is working well. ●

The author is a B.Tech in electronics and telecommunication from SRCEM, Gwalior

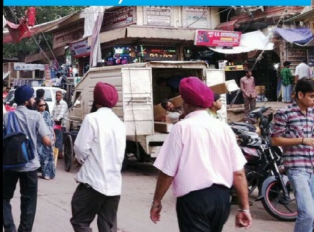**Delhi's
Lajpat Rai Market
& Bhagirath
Palace, and more...**



**Check Out
India's leading
market-places
for trade &
commerce in
electronics**

ele**B2B**.com



ElectronicsForYou
YELLOW PAGES

