

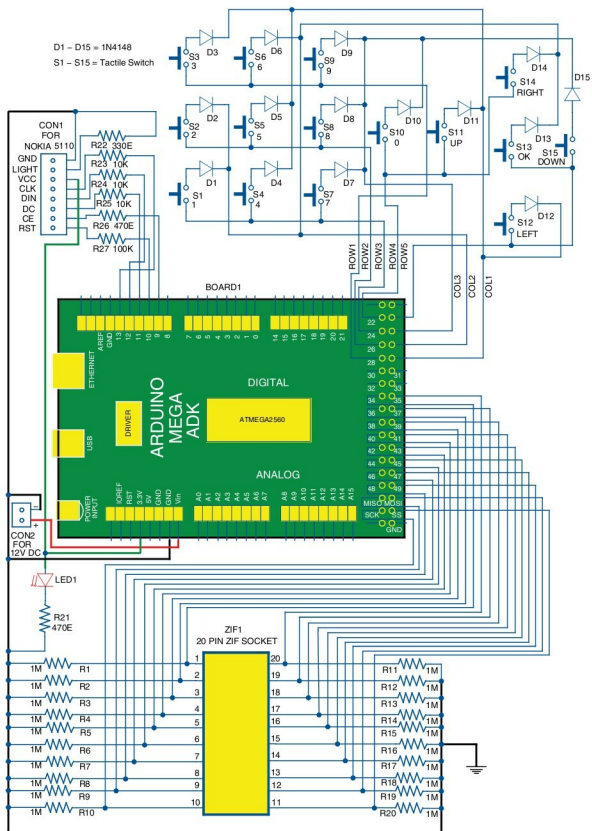


Fig. 3: Circuit diagram of the digital IC tester