

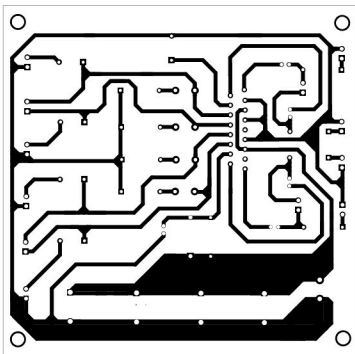


Fig. 3: Actual-size PCB pattern of the 4-channel multi-mode audio amplifier

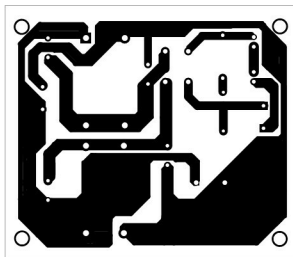


Fig. 5: Actual-size PCB pattern of the power supply circuit

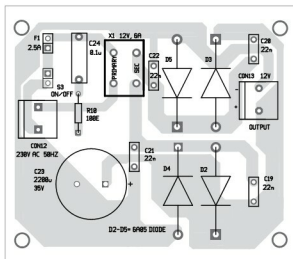


Fig. 6: Component layout of the power supply PCB

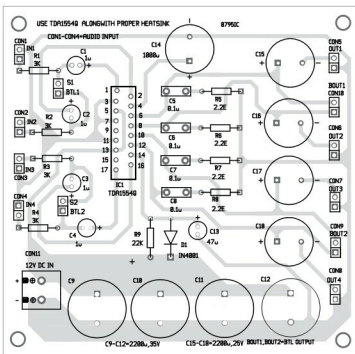


Fig. 4: Component layout of the PCB in Fig. 3

An actual-size PCB pattern for the power supply is shown Fig. 5 and its component layout in Fig. 6.

After assembling the circuit on the PCB connect 12V supply from CON13 to the amplifier circuit at

player to CON1 through CON4.

If switches S1 and S2 are open, the circuit is in single-channel mode. If closed, these are in BTL mode. The 4-channel outputs are available at CON5 through CON8.

CON11. Switch on the circuit by closing power switch S3. You can give audio inputs from any audio source like an MP3 player, laptop or DVD

Outputs for BTL mode are available at CON9 and CON10. Switch S3 and fuse F1 should be mounted on the rear panel.

It is recommended to use 2-way panel-mount spring-loaded speaker connectors for CON5 through CON10 and 3.5mm stereo female panel-mount connectors for CON1 through CON4. **EFY**



Petre Tzv Petrov was a researcher and assistant professor in Technical University of Sofia (Bulgaria) and expert-lecturer in OPFPT(Casablanca), Kingdom of Morocco. Now he is working as an electronics engineer in the private sector in Bulgaria