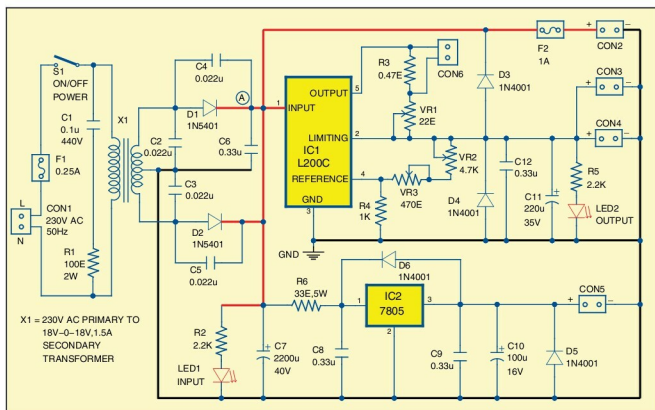


Circuit and working

The power supply is divided into two sections: adjustable, which provides adjustable output, and fixed, which provides fixed output voltage. Adjustable output voltage is provided

Diodes D3, D4, D5 and D6 protect the ICs from reverse voltages. The power supply has four outputs available at CON2 through CON5. Output at connector CON2 is a non-regulated output protected with a fuse

Outputs at CON3 and CON4 are in parallel, therefore provide same output voltage. These voltages are regulated and protected by IC1. Voltage range at that output is between 2.8V and 18V, and is almost inde-



118 NOVEMBER 2015 | ELECTRONICS FOR YOU