

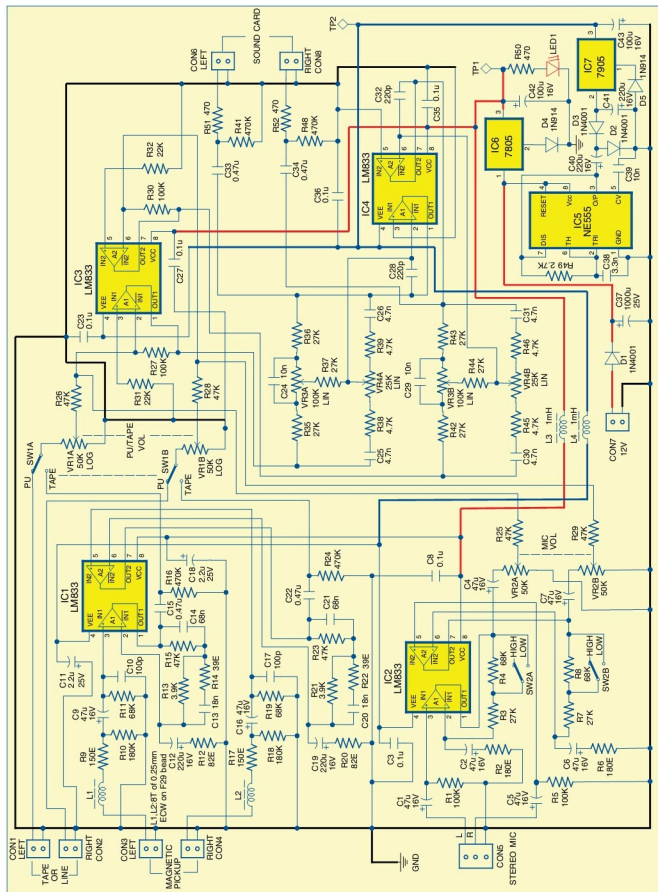


Fig. 1: Circuit diagram of the PC audio recording front end