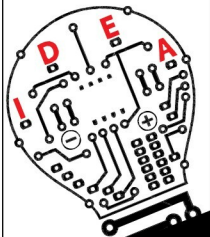


electronics
FOR YOU

Original, innovative circuit ideas are invited

from designers and
experimenters
for publication in EFY magazine



Honorarium (minimum ₹1,000)
will be paid to the contributors soon
after publication of their articles.

Complete details may be sent to the
Editor, Electronics For You,
D-87/1, Okhla Industrial Area Phase 1,
New Delhi 110020
or emailed to editsec@efy.in

For editorial guidelines, visit
http://efymag.com/Guidelines_for_EFY_authors.doc

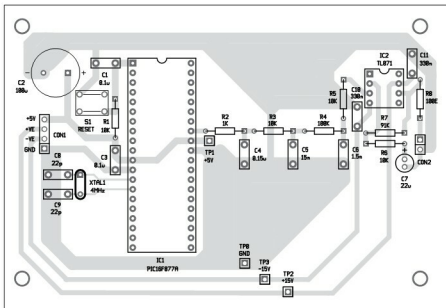


Fig. 4: Component layout of the PCB shown in Fig. 3

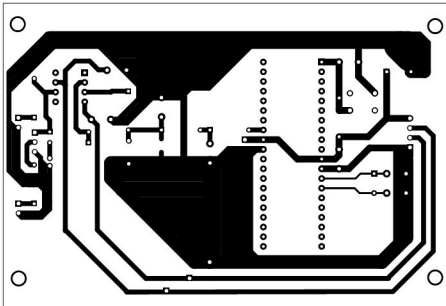


Fig. 5: Actual-size PCB pattern of the circuit for a sinusoidal signal with RC and LC filters

Test Points

Test point	Details
TP0, TP4	0V (GND)
TP1, TP5	+5.0V
TP2, TP6	+15V
TP3, TP7	-15V

to lower the resonant frequency, though it is rarely needed.

Output signal is amplified using operational amplifier IC4. The out-

put at CON5 can be adjusted with VR1. The circuits are applicable in the entire audible range of 20Hz to 20kHz.

Construction and testing

An actual-size, single-side PCB for the circuit in Fig. 1 is shown in Fig. 3 and its component layout in Fig. 4. Similarly, an actual-size, single-side PCB pattern for the circuit in Fig. 2 is shown in Fig. 5 and its component layout in Fig. 6. Ensure proper values