

Fig. 1: Circuit diagram for electronic candle

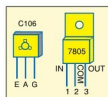


Fig. 2: Pin configurations of C106 and 7805

The random signal triggers the gate of SCR1. The electric bulb gets AC power only for the period for which SCR1 is fired.

SCR1 is fired only during the positive half cycles. Conduction of SCR1 depends upon the gate triggering pin 3 of IC2, which is random. Thus, we see a flickering effect in the light output.

Assemble the circuit on a general-purpose PCB and enclose it in a suitable

case. Fix bulb and neon bulb on the front side of the cabinet. Also, connect a power cable for giving AC mains supply to the circuit for operation. The circuit is ready to use.

Warning. Since the circuit uses 230V AC, care must be taken to avoid electric shock. ●

Launching a New Product?

Proud of Your Innovations?

Venturing into a New Domain?

Share with **ePower**

and be a
Leader!

