

Assume the first condition when the mains voltage is less than the lower set value. All the output pins (1, 18, 17,

16, 15, 14, 13, 12, 11, 10) of IC1 will be high. IC3(A) will be disabled and no step will be selected (means low volt-

age cut-off).

As the mains voltage increases to more than the lower set value, LED1

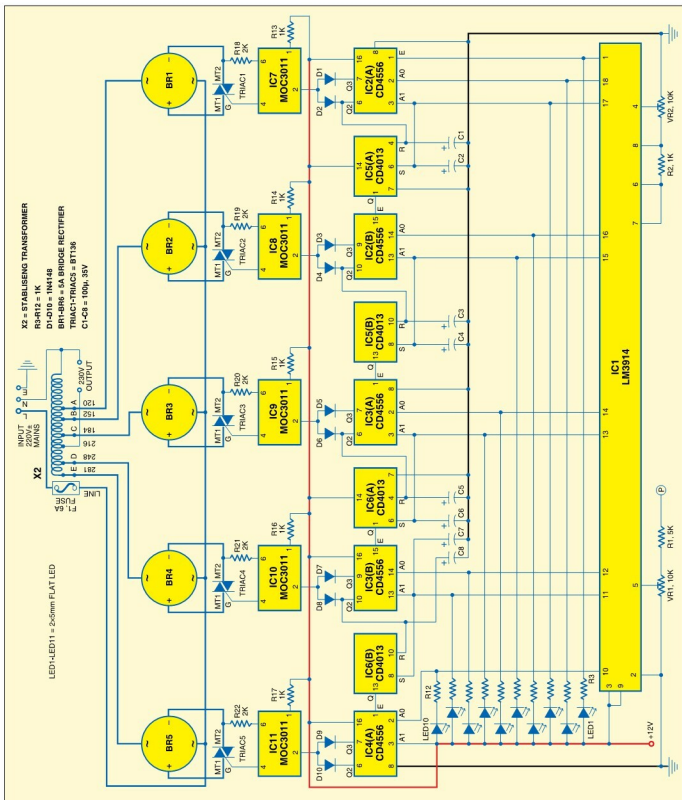


Fig. 2: Circuit diagram of voltage stabiliser