



9V supply to the oscillator, so variation in the supply voltage will not affect the frequency generated. You can also use a 12V battery to power the circuit.

Assemble the circuit on a general-purpose PCB. Install the antenna prop-

erly for maximum range.

Coils L1 through L5 are made with 20 SWG copper-enamelled wire wound over air-cores having 8mm diameter. They have 4, 6, 6, 5 and 7 turns of wire, respectively.

EFY note. This transmitter is meant only for educational purposes. Use of this transmitter with outdoor antenna is illegal in most parts of the world. The author and EFY will not be responsible for any misuse of this transmitter. ●

support@
efyindia.com

Do you have a query,
suggestion or a complaint?

You can e-mail it to
support@efyindia.com and we
will take care of the rest.