

WIRELESS WATER-LEVEL INDICATOR Without Microcontroller

PRANAV RAMESHJI ROKDE

Awired water-level indicator uses many wires, whose resistance increases as their

length increases. A wireless water-level indicator using microcontroller (MCU) is costly and not very easy

to program. Presented here is a low-cost wireless water-level indicator without an MCU.

This circuit has transmitter and receiver units. The transmitter unit is placed near the water tank, whereas the receiver unit is placed inside the house for monitoring four different levels: low, middle, full and overflow.

Circuit and working

Circuit diagram of the transmitter unit is shown in Fig. 1. It consists of 433MHz RF transmitter module TX1, an encoder HT12E (IC2), a 5V regulator 7805 (IC1), DIP switch DIP1, npn

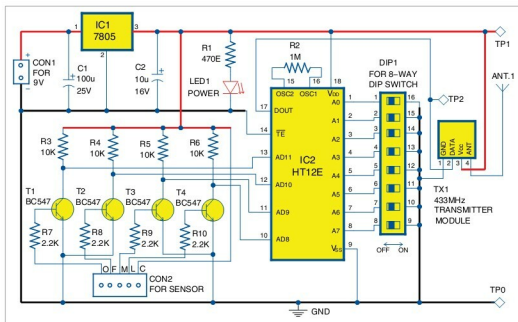


Fig. 1: Circuit diagram of transmitter unit of the wireless water-level indicator

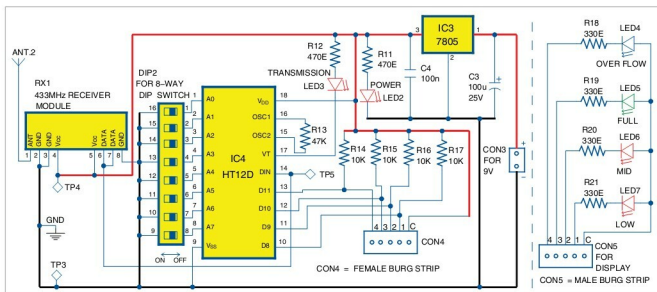


Fig. 2: Circuit diagram of receiver unit of the wireless water-level indicator