

PROGRAMMABLE POWER SUPPLY With TL431

PETRE TZV PETROV

TL431 and LM431 are relatively low-noise, stable and low-cost shunt regulators. These can be used to build all sorts of power supplies including

programmable power supplies, advantages of which are enormous. You can program the output voltage with simple switches. You can also program the output

voltage with digital codes coming from a microcontroller (MCU) or from the printer port of a PC. You can adjust any output voltage individually with resistors

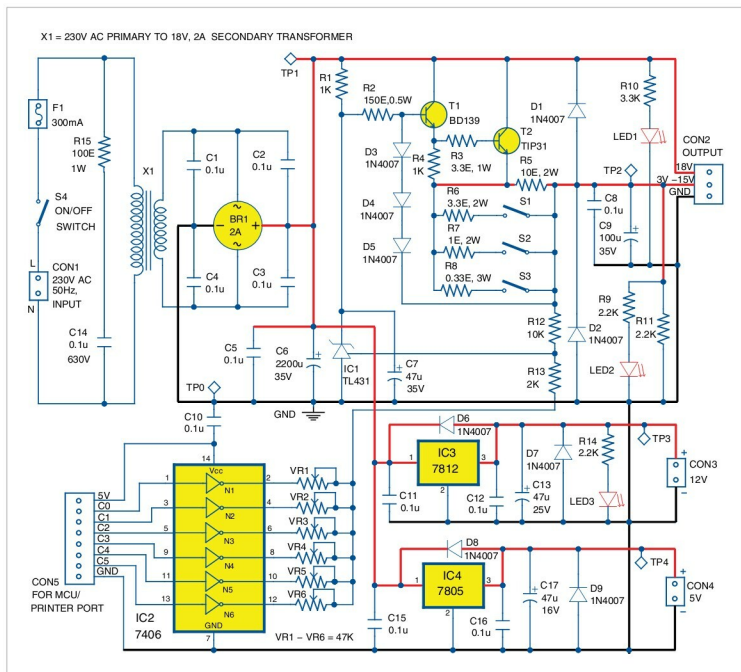


Fig. 1: Circuit diagram of the programmable power supply