



We can replace T1 and T2 with a power Darlington transistor with power dissipation of at least 75W.

Similarly, use the remaining potentiometers for required output voltages. Set the output current-limiting function by connecting S1, S2 and S3 by referring to Table II. Programmed output voltage is available at CON2. **EFY**

