

Simple Low-Cost VISITORS COUNTER

PARMARTH KANAKARAJA

Here is a simple and inexpensive visitor counter circuit that you can build easily. Visitor counters available in the market are generally expensive and are based on microcontrollers, which are difficult to program.

This circuit comprising a transmitter and a receiver can count up to

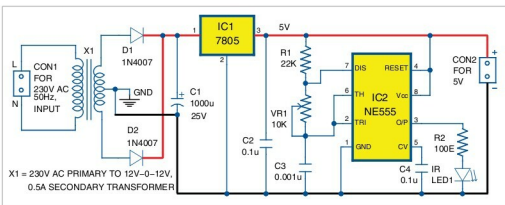


Fig. 1: Circuit of the IR transmitter unit

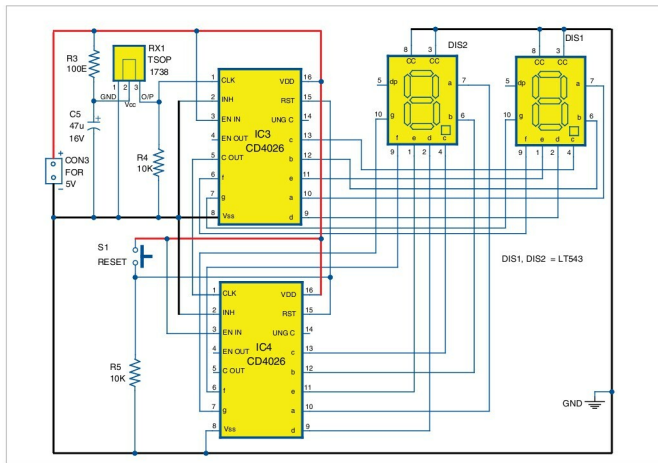


Fig. 2: Receiver unit with 7-segment displays for the visitors counter