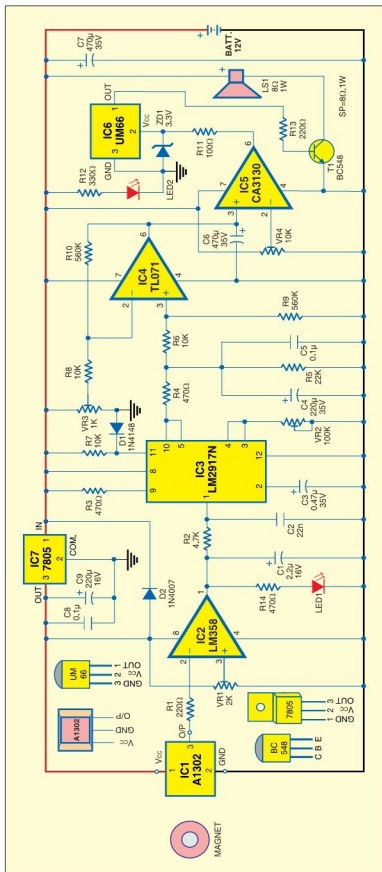


get stable output voltage.

The output of LM2917N is filtered by capacitors C4 and C5 and applied to the non-inverting input (pin 3) of low-noise op-amp TL071 (IC4). IC4 is wired as a differential amplifier to amplify the difference between its inverting and non-inverting inputs. Thus IC3 output proportional to the speed change is amplified by op-amp IC4.

The output from pin 6 of IC4 is fed to comparator CA3130 and compared with the reference voltage set at its pin 2 using preset VR4. The comparator provides regulated 3.3V (via zener diode ZD1) to music generator UM66. The output of UM66 drives speaker LS1 with the help of transistor T1, to sound an alarm whenever the two-