

Fig. 2: Actual-size PCB pattern of the circuit of the simple prescaler for transmitters

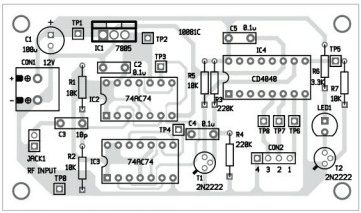


Fig. 3: Component layout of the PCB

Assemble the prescaler on the PCB shown above or on a general-purpose PCB and enclose it in a suitable case. Use a shielded cable or a thin coax for input and output connections. Mount input (CON1), output (CON2) and RF jack (JACK1) on the panel. Keep all component leads as short as possible. A 12V regulated power supply is recommended.

During testing, the prescaler performed well with an input frequency of 150MHz. Verify that test points in the circuit are as per the table before using the circuit.


To test the circuit, ensure there is 12V at test point TP1 and 5V at test point TP2 with respect to TP0, to verify the correct power supply. Now, give the RF signal using a function generator and measure the frequencies at different test points using an oscilloscope.

EFY Note. The circuit was tested successfully up to 10MHz RF frequency with around 1Vrms to 7Vrms. ●



Joy Mukherji is an electronics hobbyist and a small-business owner in Albany, New york, USA. His interests include designing RF circuits

BOSCH
Invented for life
Workshop Test Equipment for Educational Institutes
FSA 450 The multipurpose solution for measurements of the Vehicle

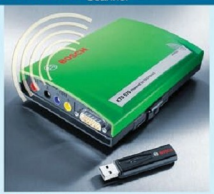Application:
• 4 channel Oscilloscope
• Ignition analyzer
• Engine analyzer
• Multimeter with digital & graphical display
KTS 570 KTS ECU Diagnostics Scanner

■ Test Equipments
• Vehicle Diagnostics
• Wheel Service
• Emission & A/C Service
■ Assembly Tools
• PT - Cordless & Electric
• PT - Penumatic
JOINT CERTIFICATION PROGRAM AVAILABLE FOR STUDENTS
For more details kindly contact
Mob: 8888816181, 9922998222
Email : avinashshendge@cyronics.com
autosolutions@cyronics.com
cyronics CYRONICS INSTRUMENTS PVT. LTD.
Corporate office:
#11, Electronic Co-op. Estate, Pune-Satara Road, Pune: 411 009. Maharashtra INDIA
Tel.: +91 20 2420 8200 Fax : +91 20 2420 8202
www.cyronics.com

