


*Fig. 3: Circuit diagram of the vibration-activated smart CRO probe*

duced at the non-inverting terminal of op-amp A1, which is greater than 1.2V at its inverting terminal. As a result, around 12V is produced at the output of A1. This is indicated by the glowing of vibration-sense indicator LED1.

The 12V produced at output of A1 charges capacitor C2 via diode D1. D1 allows the flow of current in only one direction, that is, from op-amp A1 to capacitor C2. Whenever there is a vibration, C2 charges to the maximum voltage and slowly discharges through resistor R9.

Maximum discharge time of C2 is around 30 minutes. Potmeter VR1 is used to set delay. Op-amp A2 is configured as a comparator, which compares the capacitor voltage against the set potmeter voltage. When C2 discharges, voltage decreases at the non-inverting terminal of A2. When voltage at C2

An EFY GROUP Initiative

IT'S TIME TO PROMOTE
DESIGN
IN INDIA

http://designindia.electronicsforu.com

Section launched on Electronicsforu.com to showcase design houses and innovators of India who are creating innovative electronic hardware products. If your firm has also launched or designed an innovative product for OEMs, share your details with us at editsec@efy.in.

Design IN India