

Battery

facts to check during Purchase

If the battery you're buying has been stored for over 3 months, ensure that it is recharged fully.

Remember, the open circuit voltage per cell of the battery should never go below 2.1V for the battery to work at its rated capacity and life.

To know more about choosing the right battery for your needs visit www.relicellbattery.com



VRLA and Tubular batteries

VRLA Batteries - 12V 7AH to 250 AH
Tubular Batteries - 12V 100AH to 210 AH

Part of a Rs.1000 crore IT industry group
Tested and certified by Central Power Research Institute, Bangalore (CPRI) and Electronic Test and Development Centre (STQC Directorate, Ministry of Information Technology, Govt. of India). *Download Test Certificates at www.relicellbattery.com*
UL Certified
VRLA Batteries approved and registered in DGS&D for government purchases
45 Service Centres across India

RELICELL

Greenvision Technologies Pvt.Ltd


45/1, 4th Cross, Malleswaram, Bangalore - 560 003.
Tel: +91 080 4245 9459 Fax: +91 080 4245 9460.
Email: info@relicellbattery.com

EFY Awards

Every year EFY gives away award to the best educational kit supplier in India. EFY itself supplies educational kits country-wide. But why doesn't it feature even amongst nominees in this category?

Pradeep G.
Siliconics,
Bangalore

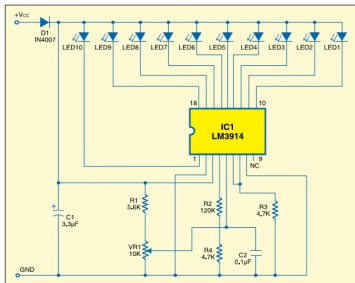EFY: Kits'n'Spares often stands first in the survey. But we cannot award ourselves!



Circuit for battery-level indicator

EFYTimes Mailers

I receive EFYTimes mailers regularly, which unfortunately don't open. Sending feedback reply doesn't help; it bounces back. I am using Internet Explorer with Gmail, and have not come across any problem so far.

M.V. Pitke

Founding Director of C-DOT

Heat Controller

Hats off to Sandeep Nair for his 'Heat Control Unit' circuit published in Aug. 2008 issue! I have successfully assembled the circuit by changing the values of resistors R1 and R2 for the temperature required in my application.

K.S. Ambirsh

Bangalore

Stereo FM Receiver

Please publish the circuit of a good-quality FM stereo receiver.

P. Pawar

Pune

Battery-level Indicator

I have assembled the 'Battery Level Indicator' circuit published in Dec. 2008 issue. As I need only the battery-level indicator section, I have removed the relay driver section which includes 230V AC mains supply, relay, transistor and 33-kilo-ohm resistor. But now

the circuit is not working. Please help.

Gauri C.

Through e-mail

The author Aniruddh Kumar Sharma replies:

You may use the circuit shown above. The voltage supplied to the circuit must be less than 35V. The brightness of the LED can be set by changing the resistor value connected at pins 6 and 7 of IC LM3914. In the given circuit, you can change the value of 4.7-kilo-ohm resistor to suit your requirement.

Wireless Device Controller

I have assembled the 'PC-based Wireless Appliance Control' project published in July 2008 issue. It's working fine in my Windows XP machine but not in Vista. What should I do to get it work in Vista? Can I use a USB-to-parallel converter for testing the circuit with my laptop?

E.R. Sai Ganesh

Hyderabad

The author Anshuman Bezborah replies:

I think it's not possible to control the parallel or serial ports in Windows Vista as it's a very secured operating system. Also, a USB-to-parallel converter might not work properly to control a device. You may try using a USB-to-serial port converter's port address in the program. It may work, but I have not tried it yet.