

Cyberstar Infocom Private Limited, New Delhi
Phone: (011) 40581611/12, 46515650,
40581604

E-mail: delhi@cyberstarindia.com
Web: www.cyberstarindia.com

Slim notebook adaptor

GlacialTech has launched a slim GlacialPower-branded notebook adaptor AC090N that doubles as a battery charger for such devices as music players and mobile phones.



On the side of the diminutive AC090N is a 5V/1A USB port, allowing you to charge batteries of the devices while running your laptop. The slim and portable AC090N is compatible with most of the laptops worldwide, and comes with a two-year warranty.

The adaptor has power efficiency above 88 per cent, maximum peak output power of 90W, universal AC input voltage of 100-240V, safety approvals including UL, CE and TUV, as well as robust protection against short-circuit, over-voltage, over-current and over-temperature.

Acro Engineering, New Delhi
Phone: (011) 40525645

Appliance protection system

Su-kam has launched a system called Power-Doc that protects your electrical appliances and electronic devices from power disturbances such as high voltage, low voltage, surges, spikes and frequency variations.



Power-Doc features zero-voltage switching, zero power consumption, voltage cut-off display and universal plug-in. Zero-voltage switching enables longevity of appliances and zero power consumption helps in reducing energy consumption by 11.5 per cent every month. Voltage cut-off display rescues electrical appliances from breakdown and restores power supply automatically.

Su-Kam Power Systems Ltd, Gurgaon
Fax: (0124) 4038700
Phone: 4030700, 4170500
E-mail: info@su-kam.com
Web: www.su-kam.com

Voltage controller

Applied Electricals & Electronics has introduced a high-quality and cost-effective microServo voltage controller that reduces production overheads like wiring and testing when put on the



servo voltage stabiliser. It greatly reduces labour costs and increases the production rate of voltage stabilisers.

The unit is designed with innovative software algorithms residing on latest-technology PIC microcontroller chips. It has a built-in driver, which fully controls AC synchronous servo motor, and protections from under-voltage, over-voltage and overload with time delays. It displays output voltage, input voltage, load current and frequency. Manual mode is especially built for field testing.

Applied Electricals & Electronics, New Delhi
E-mail: info@aeindia.com
Web: www.aeindia.com

COMPONENTS

Low-noise VCXOs

ON Semiconductor has introduced the PureEdge family of silicon-based voltage-controlled crystal oscillators (VCXOs). Offering reduced costs, and ultra-low jitter and phase noise versus alternative solutions available on the

market, the NBVSBAxxx series is ideal for providing low-jitter, stable reference clock in networking, SONET, 10 Gigabit Ethernet, base stations and broadcasting equipment.

The devices meet the requirements of 2.5V and 3.3V low-voltage positive emitter-coupled logic clock generation applications offering a low jitter (0.5ps) reference clock. The ability to power the devices with either a 2.5V or 3.3V supply enables design flexibility and simplifies the product's bill-of-materials driving further system cost reduction. The tri-state enable/disable feature allows the user to turn the output on and off across the entire industrial temperature range of -40°C to +85°C.

Arrow Electronics India Private Ltd, New Delhi
Phone: (011) 45045500

-36V, 200mA LDO voltage regulators

Texas Instruments claims to have introduced the industry's first -36V low-dropout (LDO) regulators. The TPS7A30, paired with the positive-voltage TPS7A49, provides designers with a total solution for powering precision analogue applications. The devices feature ultra-high power supply rejection ratio (PSRR) performance

and as low as 16 μ Vrms of output noise. The TPS7A30 generates 200 mA, while the TPS7A49 manages 150 mA.

Customers designing high-precision equipment need clean bipolar power rails for powering operational amplifiers, analogue-to-digital converters or digital-to-analogue converters. The TPS7A30 and TPS7A49 help meet that requirement with wide input voltages, lowest noise and maximum amount of transient headroom.

Texas Instruments (India) Pvt Ltd, Bengaluru
Fax: (080) 25048286
Phone: 25099221
Web: www.ti.com

